



Electrical Subsystem

Digital Circuits using Verilog


By **Puja Naga Prasanna**

Mentor: **Nikhil**


Co-Mentor: **Tanmay**

Verilog:

 A Hardware Description Language (HDL) to describe digital circuits.



Simple Digital Circuit

 


Aim:

To learn Verilog(HDL), implement a simple circuit
& to solve a problem using the simple circuit




Part-A:

To design a mod-n counter in Verilog

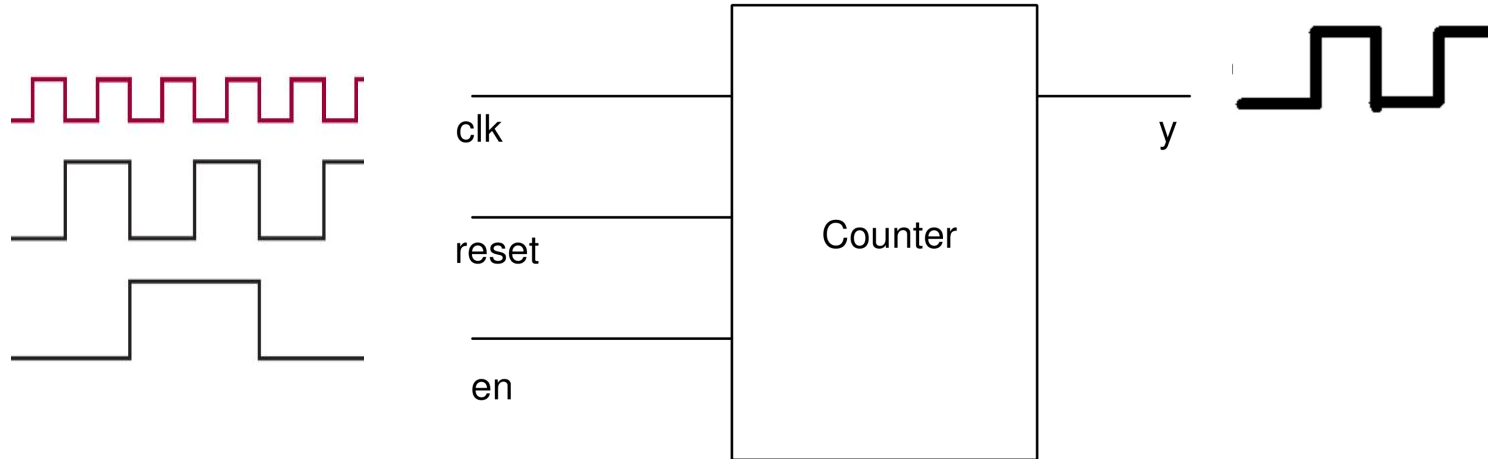


Mod-n counter:

 

Part-B:


To solve a design problem

Waveform:

 


NOTE: The split in waveform here is used to indicate that it repeats for a long period of time.

 - Circuit registers multiple button presses for a single press




Counting no.of button presses

 


*Checks prev & present value of btn & increases count

Button Output (without Mod-n counter)

 


*Checks prev & present value of btn

Button Output (using Mod-n counter)


 


 If a person intentionally press the button for long time how will it return output?



Multiple photos for one click

A long button press

  

Week1

- Started with Verilog
- Installed Vivado software
- Ref: <https://www.nandland.com/verilog/tutorials/index.html>

Verilog Tutorials

- [Introduction To Verilog for beginners with code examples](#)
- [Always Blocks for beginners](#)
- [Your First Verilog Program: An LED Blinker](#)
- [Recommended Coding Style for Verilog](#)

Week 2&3



- Finished the counter description
- Found potential solution for design problem


**Verilog description of above problems:*

<https://drive.google.com/drive/folders/1EcUGWLFiv1lnILN0XWHiXGRrb1gPZbTi?usp=sharing>

Simulation Errors:

  ⤴ [Vivado 12-4473] Detected error while running simulation. Please correct the issue and retry this operation.



 

TEAMWORK



Time Management



